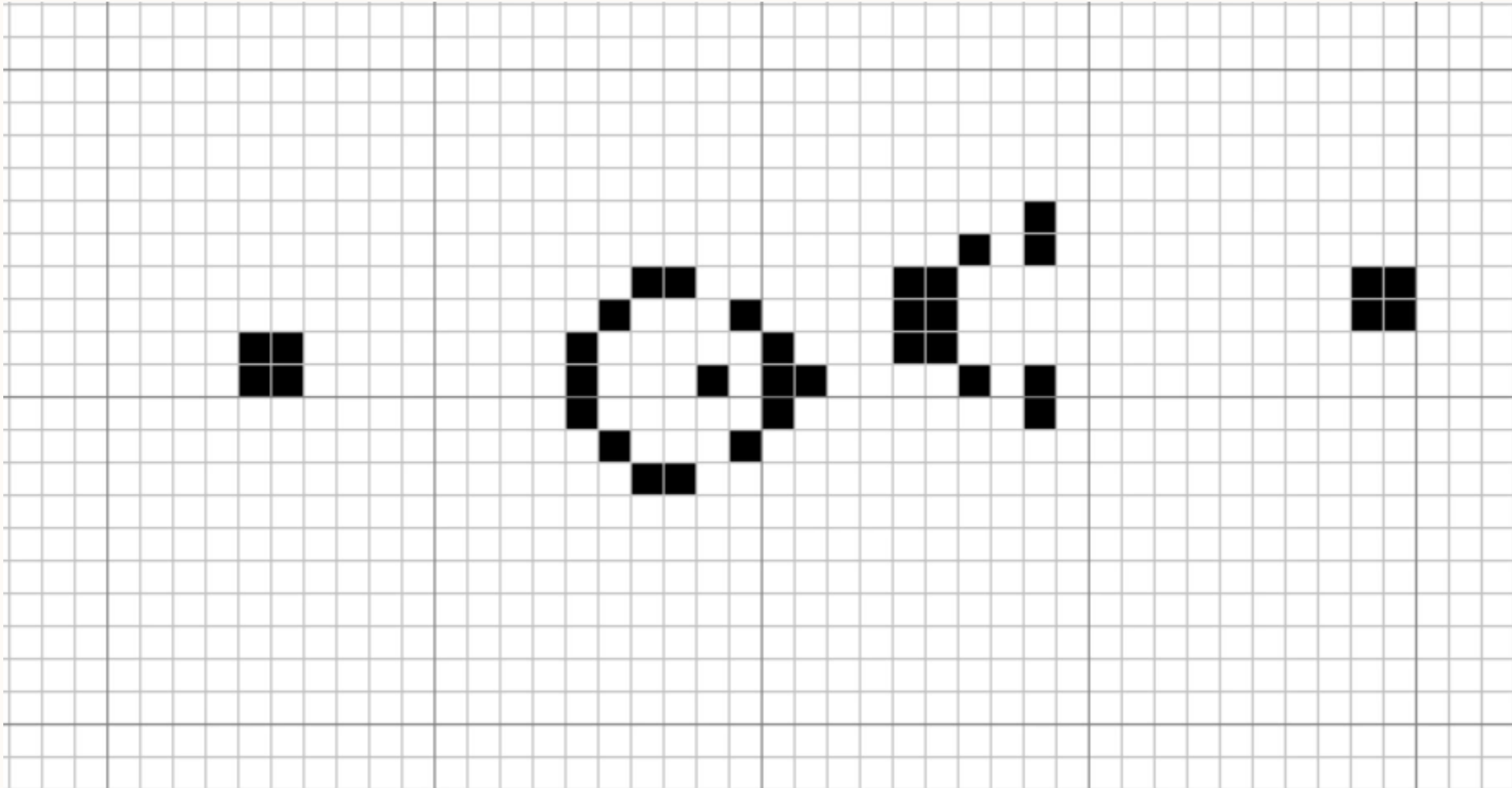


WORKSHOP 1

COMSM1302 Overview of Computer Architecture

Kira Clements, University of Bristol

CONWAY'S GAME OF LIFE




MODIFIED GAME OF LIFE

In this modified Game of Life, there are only 2 rules:

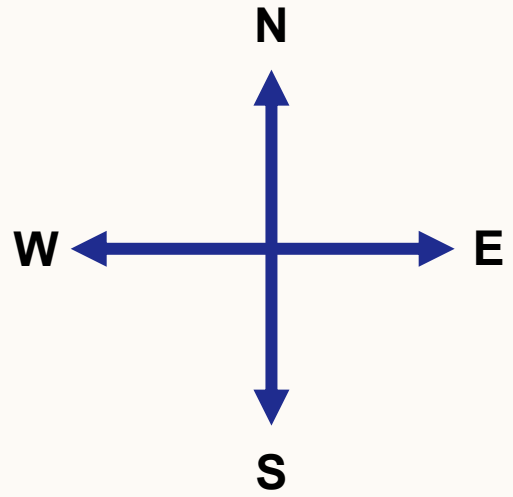1. **Birth/Survival:** an uninhabited cell becomes inhabited, and an inhabited cell stays inhabited, if exactly 3 of its adjacent neighbours are inhabited.
2. **Death:** an inhabited cell becomes uninhabited, and an uninhabited cell stays uninhabited, if the number of inhabited adjacent neighbours is *not* exactly 3.

We define “adjacent neighbours” to be cells directly above, below, left, and right of the cell.

Create a circuit that outputs whether an individual cell will be uninhabited or inhabited next.



0 = uninhabited

1 = inhabited

| N | E | S | W | Cell |
|---|---|---|---|------|
| 0 | 0 | 0 | 0 | 0 |
| 0 | 0 | 0 | 1 | 0 |
| 0 | 0 | 1 | 0 | 0 |
| 0 | 0 | 1 | 1 | 0 |
| 0 | 1 | 0 | 0 | 0 |
| 0 | 1 | 0 | 1 | 0 |
| 0 | 1 | 1 | 0 | 0 |
| 0 | 1 | 1 | 1 | 1 |
| 1 | 0 | 0 | 0 | 0 |
| 1 | 0 | 0 | 1 | 0 |
| 1 | 0 | 1 | 0 | 0 |
| 1 | 0 | 1 | 1 | 1 |
| 1 | 1 | 0 | 0 | 0 |
| 1 | 1 | 0 | 1 | 1 |
| 1 | 1 | 1 | 0 | 1 |
| 1 | 1 | 1 | 1 | 0 |

| NE\SW | 00 | 01 | 11 | 10 |
|-------|----|----|----|----|
| 00 | 0 | 0 | 0 | 0 |
| 01 | 0 | 0 | 1 | 0 |
| 11 | 0 | 1 | 0 | 1 |
| 10 | 0 | 0 | 1 | 0 |

$$(\neg N \wedge E \wedge S \wedge W) \vee (N \wedge \neg E \wedge S \wedge W) \vee (N \wedge E \wedge \neg S \wedge W) \vee (N \wedge E \wedge S \wedge \neg W)$$

$$(\neg N \wedge E \wedge S \wedge W) \vee (N \wedge \neg E \wedge S \wedge W) \vee (N \wedge E \wedge \neg S \wedge W) \vee (N \wedge E \wedge S \wedge \neg W)$$

$$(((\neg N \wedge E) \vee (N \wedge \neg E)) \wedge (S \wedge W)) \vee (N \wedge E \wedge \neg S \wedge W) \vee (N \wedge E \wedge S \wedge \neg W)$$

$$(((\neg N \wedge E) \vee (N \wedge \neg E)) \wedge (S \wedge W)) \vee ((N \wedge E) \wedge ((\neg S \wedge W) \vee (S \wedge \neg W)))$$

$$((N \oplus E) \wedge (S \wedge W)) \vee ((N \wedge E) \wedge ((\neg S \wedge W) \vee (S \wedge \neg W)))$$

$$((N \oplus E) \wedge (S \wedge W)) \vee ((N \wedge E) \wedge (S \oplus W))$$

Let's compare creating circuits based on our original expression and our last expression...